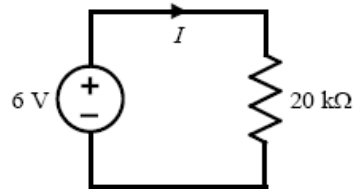


Exercícios retirados do livro: Basic Engineering Circuit Analysis, 7Ed.

Problem 2.1

Find the current I and the power supplied by the source in the network shown.




Suggested Solution

$$I = \frac{6}{20 \times 10^3} = 0.3 \text{ mA}$$

$$P = VI = (6)(0.3 \times 10^{-3}) = 1.8 \text{ mW}$$

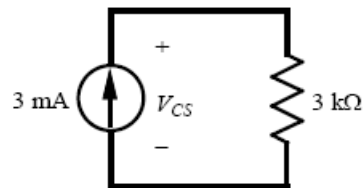Problem 2.2

In the circuit shown, find the voltage across the current source and the power absorbed by the resistor.




Suggested Solution

$$V_{CS} = (3 \times 10^{-3})(3 \times 10^3) = 9 \text{ V}$$

$$P = VI = (3 \times 10^{-3})(9) = 27 \text{ mW}$$

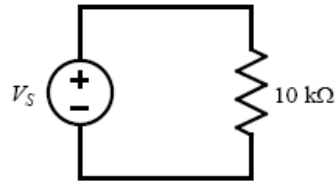Problem 2.3

If the $10\text{-k}\Omega$ resistor in the network shown absorbs 2.5 mW , find V_S .




Suggested Solution

$$P = \frac{V_S^2}{10\text{ k}\Omega}$$

$$\text{or } V_S = \sqrt{P \times R} = \sqrt{(2.5 \times 10^{-3})(10 \times 10^3)} = 5\text{ V}$$

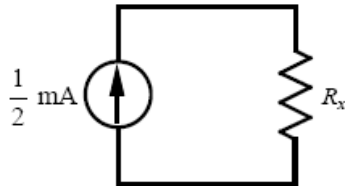Problem 2.4

In the network shown, the power absorbed by R_x is 5 mW . Find R_x .




Suggested Solution

$$R_x = \frac{P}{I^2} = \frac{5 \times 10^{-3}}{(0.5 \times 10^{-3})^2} = 20\text{ k}\Omega$$

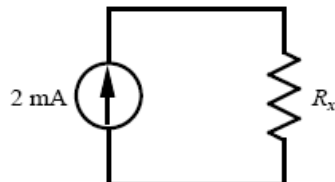Problem 2.5

In the network shown, the power absorbed by R_x is 20 mW . Find R_x .




Suggested Solution

$$R = \frac{P}{I^2} = \frac{20 \times 10^{-3}}{(2 \times 10^{-3})^2} = 5\text{ k}\Omega$$

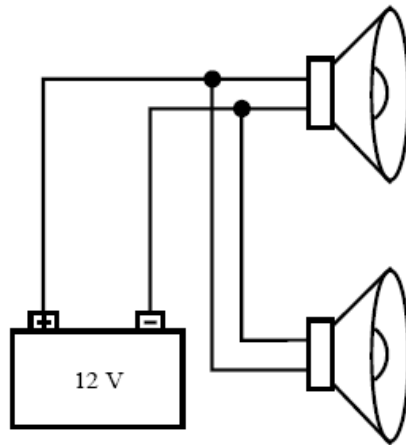Problem 2.7

An automobile uses two halogen headlights connected as shown. Determine the power supplied by the battery if each headlight draws 3 A of current.




Suggested Solution


$$P_s = VI = (12)(3 + 3) = 72 \text{ W}$$

Problem 2.9

Find I_1 in the network shown.

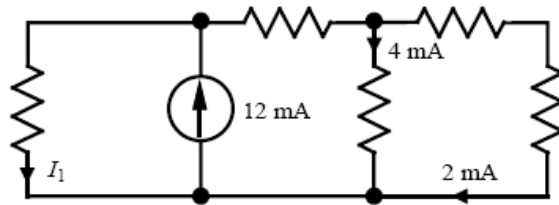

Suggested Solution

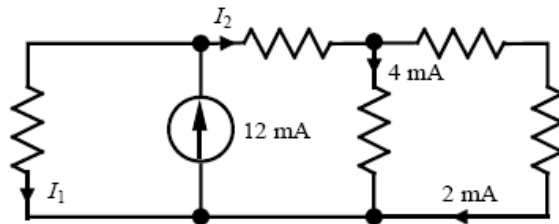


$$I_2 = 0.004 + 0.002 = 0.006 \text{ A}$$

$$0.012 = I_1 + I_2$$

Problem 2.25

Find V_x in the circuit shown.

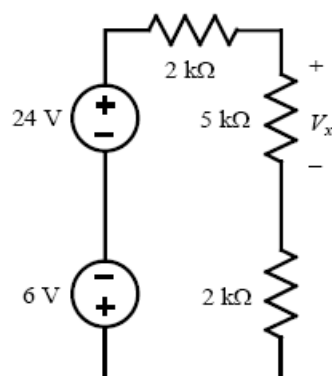


Suggested Solution

Using voltage division,

$$V_x = \left(\frac{5000}{2000 + 5000 + 2000} \right) (24 - 6) = 10 \text{ V}$$

Problem 2.26

Find V_x in the circuit shown.

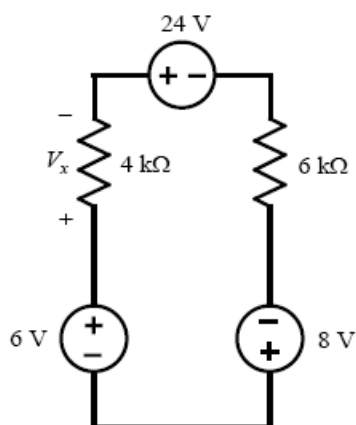


Suggested Solution

Using voltage division,

$$V_x = \left(\frac{4000}{4000 + 6000} \right) (6 + 8 - 24) = -4 \text{ V}$$

Problem 2.31

Find I_o in the circuit shown.

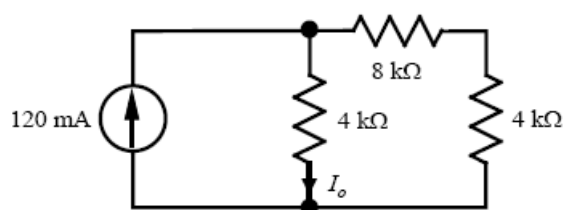


Suggested Solution

Using current division,

$$I_o = \left[\frac{\frac{1}{4000}}{\frac{1}{4000} + \frac{1}{8000 + 4000}} \right] (0.120) = 90 \text{ mA}$$


Problem 2.33

Find V_o in the circuit shown.

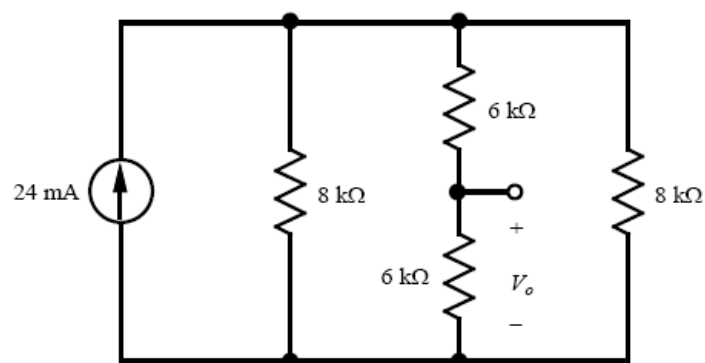

Suggested Solution

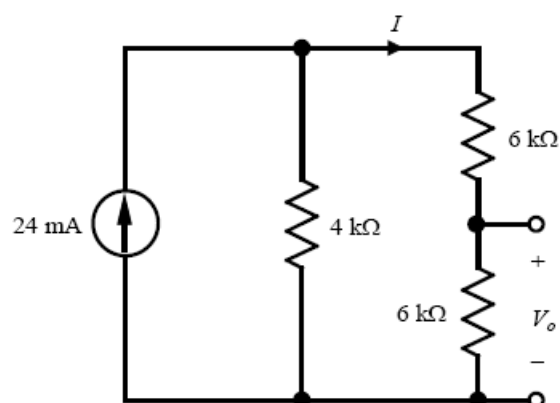Combining the 8-k Ω resistors in parallel yields the following circuit.



Using current division,


$$I = \left(\frac{\frac{1}{6000 + 6000}}{\frac{1}{4000} + \frac{1}{6000 + 6000}} \right) (0.024) = 6 \text{ mA}$$

Then,

$$V_o = 6000 I = 36 \text{ V}$$


Problem 2.37

Find R_{AB} in the circuit shown.

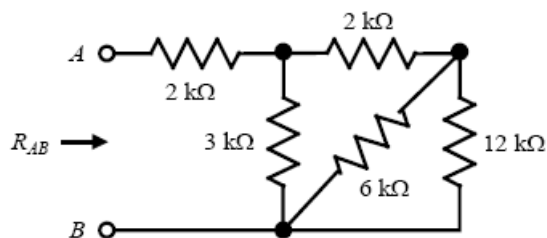

Suggested Solution

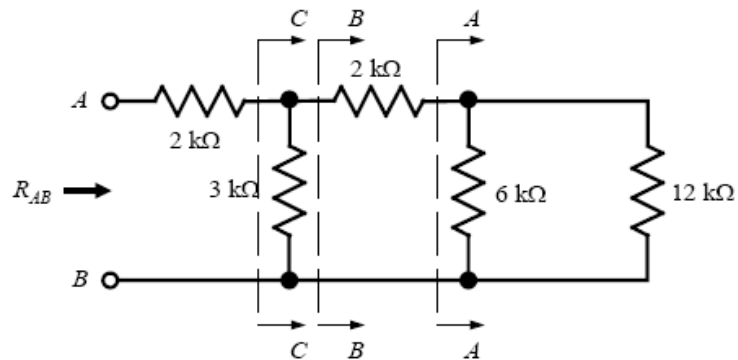The network can be redrawn as shown below.



Then,

At A-A: $6000 \parallel 12000 = 4 \text{ k}\Omega$

At B-B: $2000 + 4000 = 6 \text{ k}\Omega$


At C-C: $3000 \parallel 6000 = 2 \text{ k}\Omega$

and


$R_{AB} = 2000 + 2000 = 4 \text{ k}\Omega$

Problem 2.38

Find R_{AB} in the circuit shown.

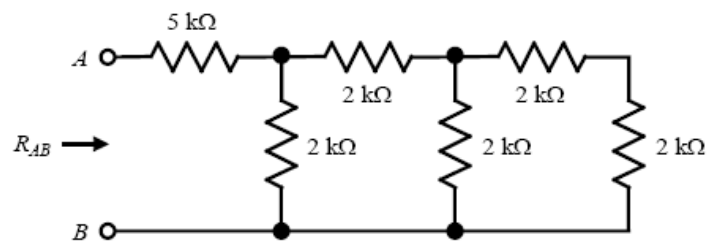

Suggested Solution

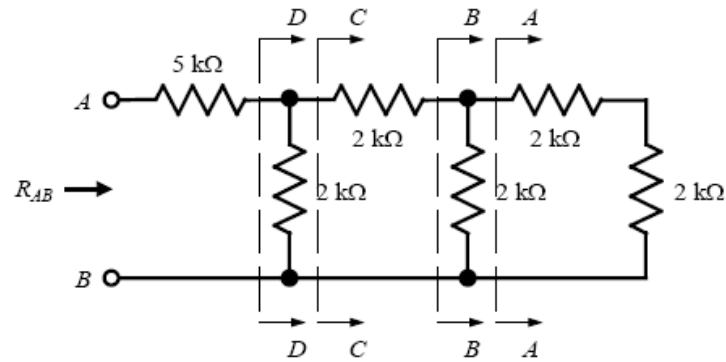

At A-A: $2000 + 2000 = 4 \text{ k}\Omega$

At B-B: $2000 \parallel 4000 = \frac{4}{3} \text{ k}\Omega$

At C-C: $2000 + \frac{4000}{3} = \frac{10}{3} \text{ k}\Omega$


At D-D: $2000 \parallel \frac{10000}{3} = 1250 \text{ }\Omega$

Then,

$R_{AB} = 5000 + 1250 = 6250 \text{ }\Omega$


Problem 2.39

Find R_{AB} in the network shown.

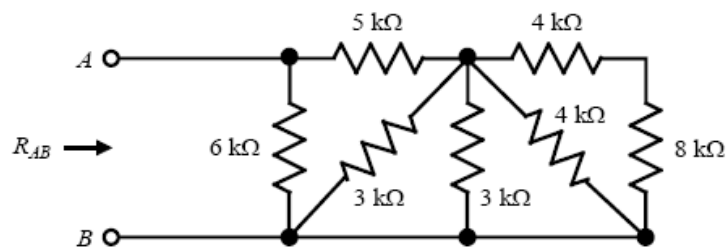

Suggested Solution

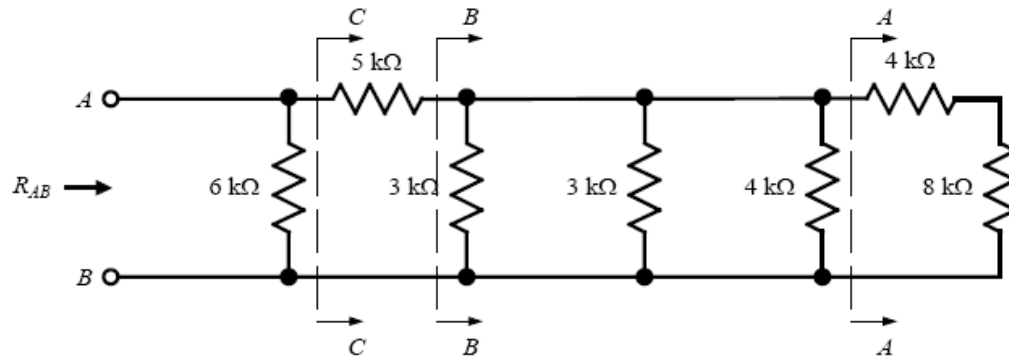The network can be redrawn as shown below.



At $A-A$: $4000 + 8000 = 12 \text{ k}\Omega$

At $B-B$: $3000 \parallel 3000 \parallel 4000 \parallel 12000 = 1 \text{ k}\Omega$


At $C-C$: $5000 + 1000 = 6 \text{ k}\Omega$

Therefore,

$R_{AB} = 6000 \parallel 6000 = 3 \text{ k}\Omega$


Problem 2.40

Find R_{AB} in the circuit shown.

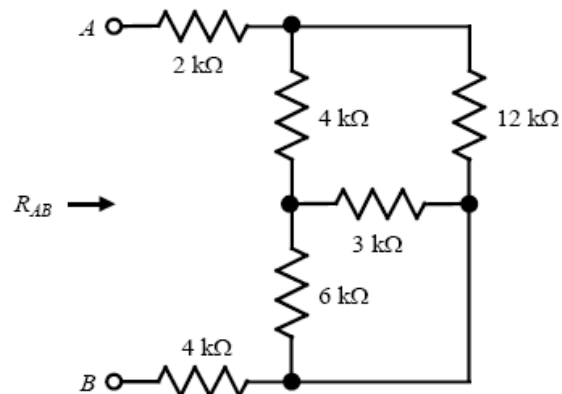

Suggested Solution

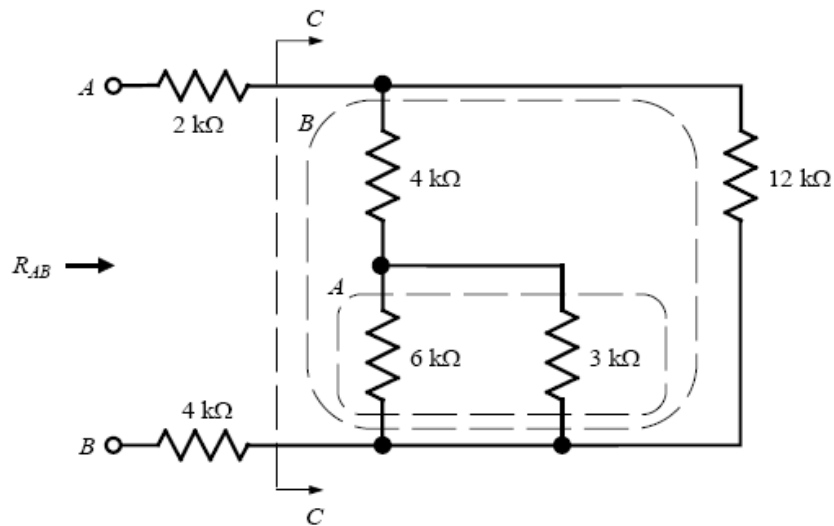The circuit can be redrawn as shown below.



At A : $6000 \parallel 3000 = 2 \text{ k}\Omega$

At B : $4000 + 2000 = 6 \text{ k}\Omega$


At C - C : $6000 \parallel 12000 = 4 \text{ k}\Omega$

Then,

$$R_{AB} = 2000 + 4000 + 4000 = 10 \text{ k}\Omega$$


Problem 2.43

Find R_{AB} in the circuit shown.

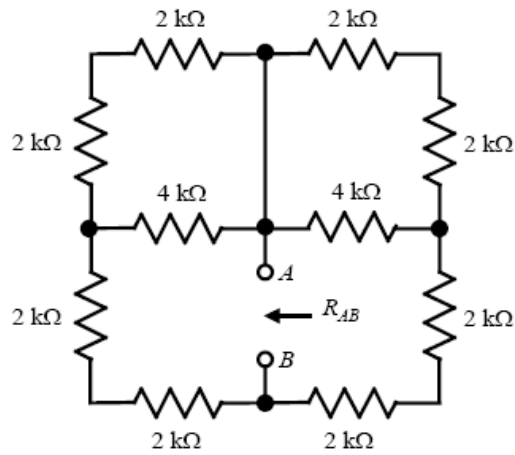


Suggested Solution

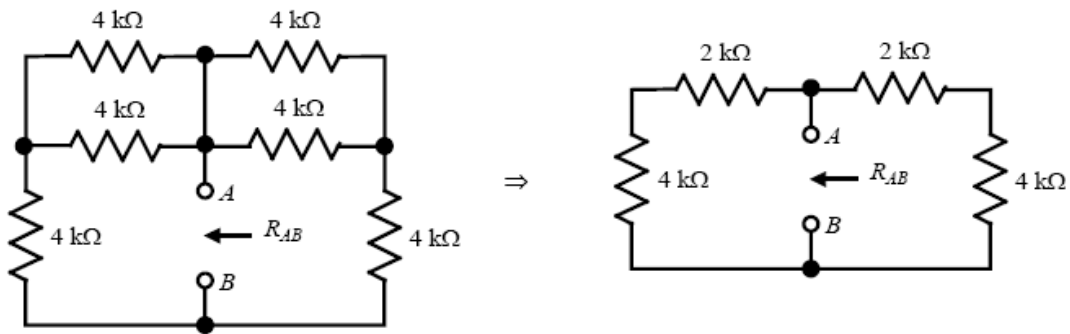Combining each series pair of 2-k Ω resistors, the circuit can be redrawn as follows:



or

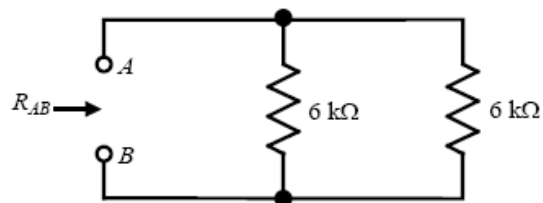


Then,

$$R_{AB} = 6000 \parallel 6000 = 3 \text{ k}\Omega$$

Problem 2.48

Find I_1 and V_o in the circuit shown.

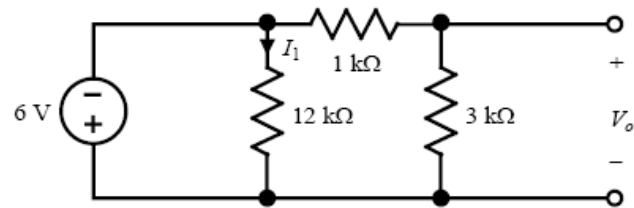


Suggested Solution

From Ohm's Law:
$$I_1 = \frac{-6 \text{ V}}{12 \text{ k}\Omega} = -0.5 \text{ mA}$$

By application of voltage division:
$$V_o = \left(\frac{3 \text{ k}\Omega}{3 \text{ k}\Omega + 1 \text{ k}\Omega} \right) (-6 \text{ V}) = -4.5 \text{ V}$$


Problem 2.49

Find I_1 and V_o in the circuit shown.

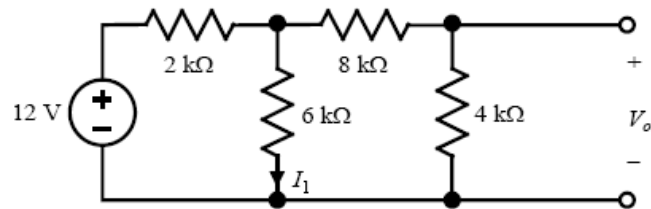

Suggested Solution

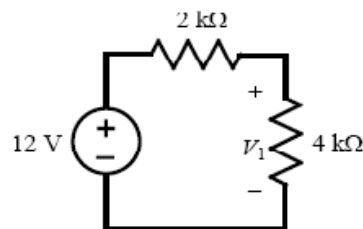
Combining resistors $\left[6 \text{ k}\Omega \parallel (8 \text{ k}\Omega + 4 \text{ k}\Omega) = 4 \text{ k}\Omega \right]$ reduces the network to the following:



Using voltage division, then

$$V_1 = \left(\frac{4000}{2000 + 4000} \right) (12 \text{ V}) = 8 \text{ V}.$$

Looking back at the original circuit,

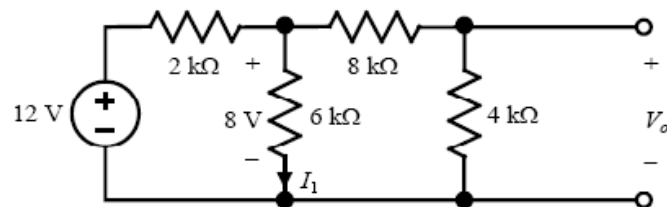


Ohm's Law:
$$I_1 = \frac{8 \text{ V}}{6 \text{ k}\Omega} = \frac{4}{3} \text{ mA}$$

Voltage division:
$$V_o = \left(\frac{4000}{8000 + 4000} \right) (8) = \frac{8}{3} \text{ V}$$

~


Problem 2.52

Find V_o in the network shown.

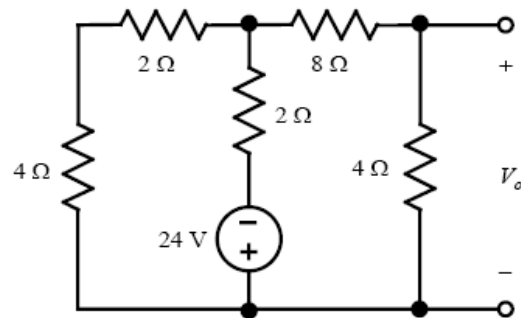


Suggested Solution

The network can be redrawn as:

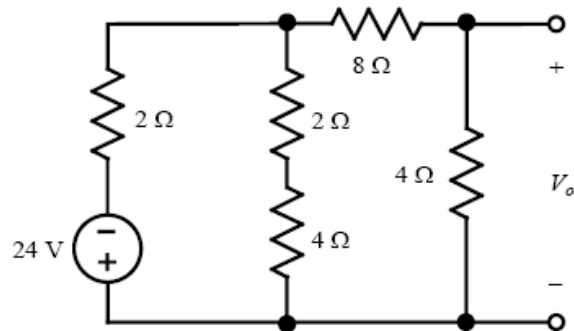


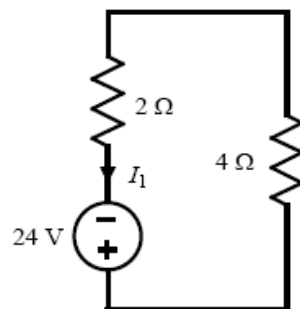Combining the four resistors on the right-hand side $\left[(4\ \Omega + 2\ \Omega) \parallel (8\ \Omega + 4\ \Omega) = 4\ \Omega \right]$ yields:



and $I_1 = \frac{24\ \text{V}}{(2\ \Omega + 4\ \Omega)} = 4\ \text{A}.$

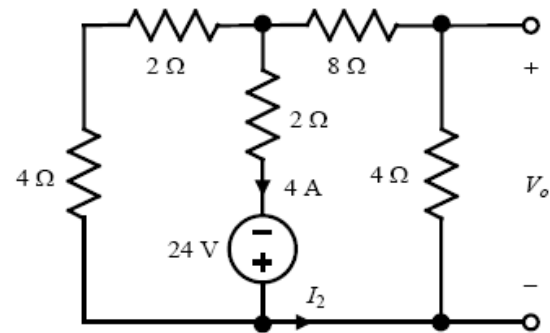Then, reconsidering the original circuit,




$$I_2 = \left[\frac{(4+2)}{(4+2)+(8+4)} \right] (4 \text{ A}) = \frac{4}{3} \text{ A}$$

and

$$V_o = -(4 \text{ A}) \left(\frac{4}{3} \text{ A} \right) = -\frac{16}{3} \text{ V}$$


Problem 2.53

Find I_o in the circuit shown.

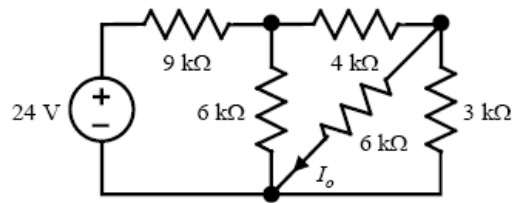

Suggested Solution


The circuit can be redrawn as:

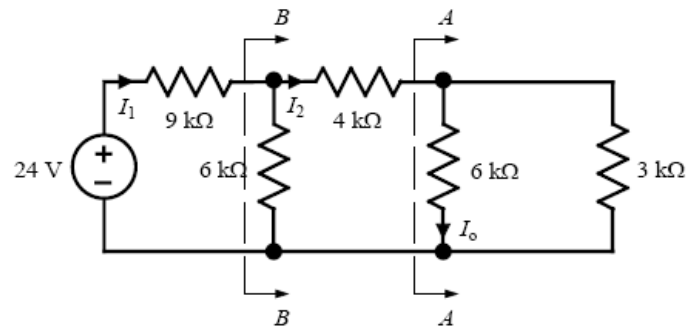

At A-A: $6000 \parallel 3000 = 2 \text{ k}\Omega$

At B-B: $6000 \parallel (4000 + 2000) = 3 \text{ k}\Omega$

The circuit simplifies to:

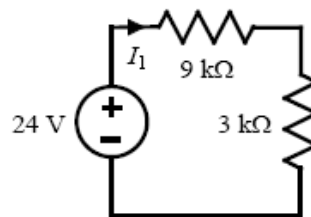


$$\text{Then, } I_1 = \frac{24}{9000 + 3000} = 2 \text{ mA} \Rightarrow I_2 = \left[\frac{6000}{6000 + (4000 + 2000)} \right] I_1 = 1 \text{ mA}$$

$$\text{and } I_o = \left(\frac{3000}{3000 + 6000} \right) I_2 = \frac{1}{3} \text{ mA} .$$


Problem 2.57

Find I_o in the circuit shown.

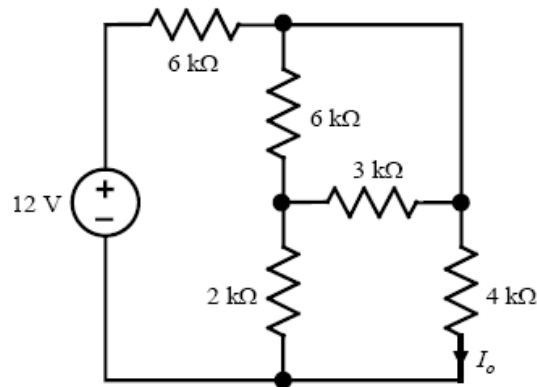

Suggested Solution

The circuit can be redrawn as:

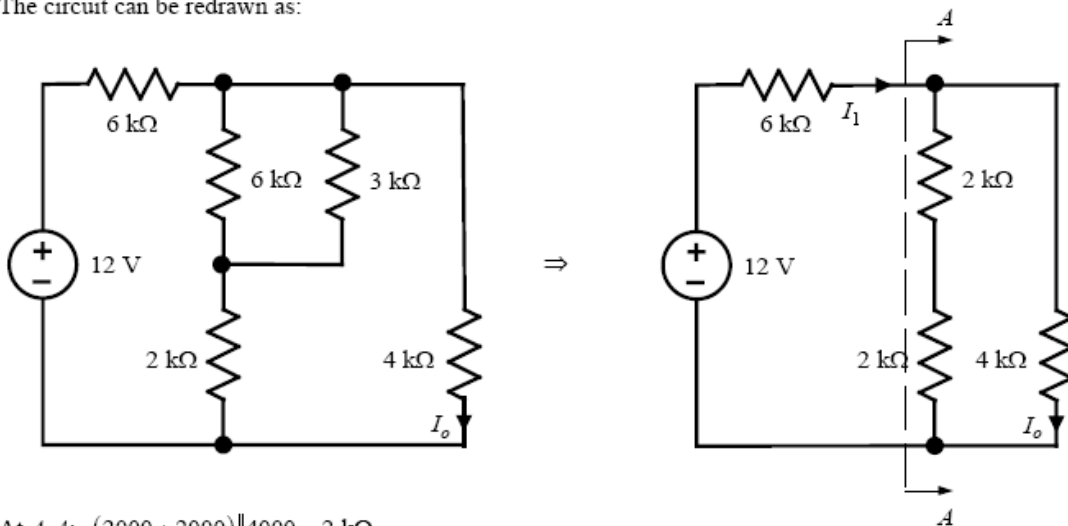


At A-A: $(2000 + 2000) \parallel 4000 = 2 \text{ k}\Omega$

$$I_1 = \frac{12}{6000 + 2000} = 1.5 \text{ mA}$$


$$\text{Using current division, } I_o = \left[\frac{(2000 + 2000)}{(2000 + 2000) + 4000} \right] I_1 = 0.75 \text{ mA}$$

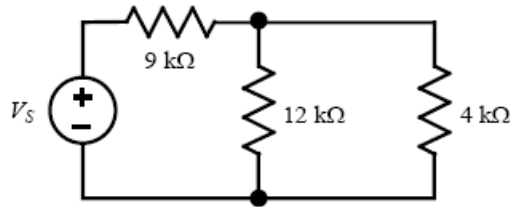Problem 2.60

If the power absorbed by the $4\text{-k}\Omega$ resistor in the circuit shown is 36 mW , find V_S .



Suggested Solution

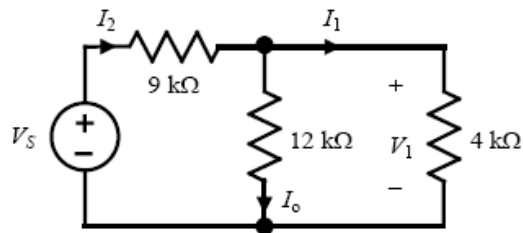

$$P_{4\text{ k}\Omega} = 36\text{ mW} = \frac{V_1^2}{4000} \Rightarrow V_1 = 12\text{ V}$$

$$I_o = \frac{V_1}{12\text{ k}\Omega} = 1\text{ mA}$$


$$I_1 = \frac{V_1}{4\text{ k}\Omega} = 3\text{ mA}$$

$$I_2 = I_o + I_1 = 1\text{ mA} + 3\text{ mA} = 4\text{ mA}$$


$$V_S = (9\text{ k}\Omega)I_2 + V_1 = 48\text{ V}$$

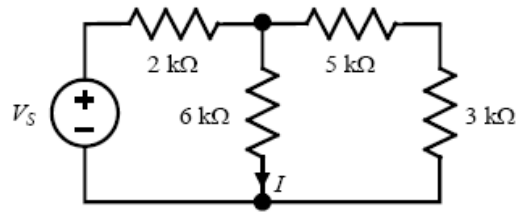Problem 2.63

In the circuit shown, $I = 4 \text{ mA}$. Find V_S .



Suggested Solution

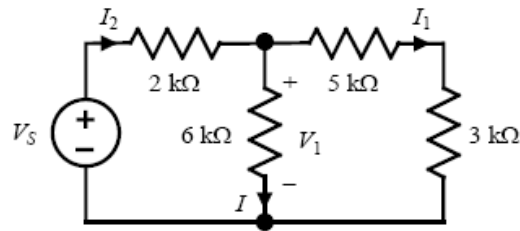

$$V_1 = (6 \text{ k}\Omega)I = 24 \text{ V}$$


$$I_1 = \frac{V_1}{5 \text{ k}\Omega + 3 \text{ k}\Omega} = \frac{24}{8000} = 3 \text{ mA}$$

$$I_2 = I + I_1 = 0.004 + 0.003 = 7 \text{ mA}$$


$$V_S = (2 \text{ k}\Omega)I_2 + V_1 = 14 + 24 = 38 \text{ V}$$

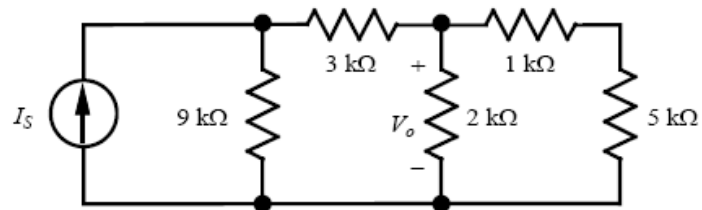Problem 2.67

In the network shown, $V_o = 6 \text{ V}$. Find I_S .



Suggested Solution

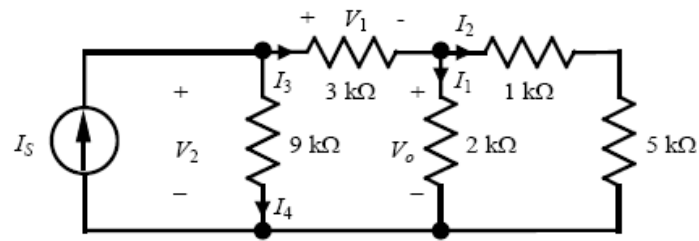

$$I_1 = \frac{V_o}{2 \text{ k}\Omega} = \frac{6}{2000} = 3 \text{ mA}$$

$$I_2 = \frac{V_o}{1 \text{ k}\Omega + 5 \text{ k}\Omega} = \frac{6}{6000} = 1 \text{ mA}$$

$$I_3 = I_1 + I_2 = 0.003 + 0.001 = 4 \text{ mA}$$

$$V_1 = (3 \text{ k}\Omega) I_3 = 12 \text{ V}$$


$$V_2 = V_1 + V_o = 12 + 6 = 18 \text{ V}$$

$$I_4 = \frac{V_2}{9 \text{ k}\Omega} = \frac{18}{9000} = 2 \text{ mA}$$


$$I_S = I_3 + I_4 = 0.004 + 0.003 = 6 \text{ mA}$$

Problem 2.71

Find V_o in the circuit shown.

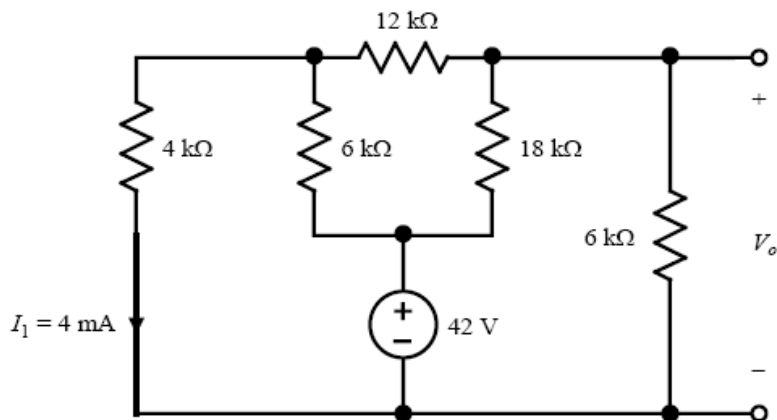

Suggested Solution

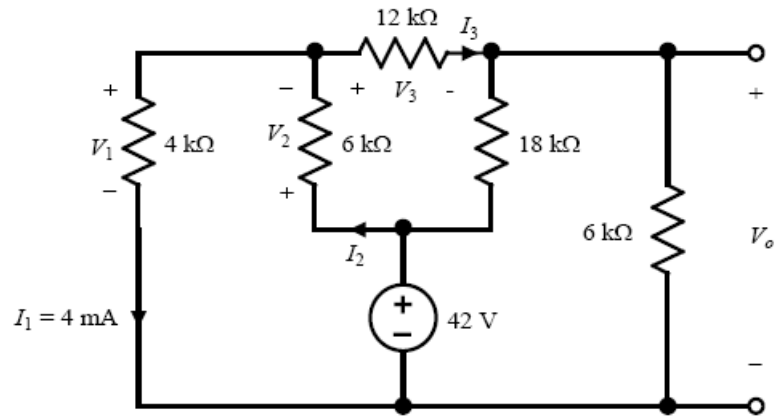

$$V_1 = (4 \text{ k}\Omega) I_1 = 16 \text{ V}$$

$$V_2 = 42 \text{ V} - V_1 = 42 - 16 = 26 \text{ V}$$

$$I_2 = \frac{V_2}{6 \text{ k}\Omega} = \frac{26}{6000} = \frac{13}{3} \text{ mA}$$


$$I_3 = I_2 - I_1 = \frac{13}{3} \text{ mA} - 4 \text{ mA} = \frac{1}{3} \text{ mA}$$

$$V_3 = (12 \text{ k}\Omega) I_3 = 4 \text{ V}$$

$$V_o = V_1 - V_3 = 16 - 4 = 12 \text{ V}$$

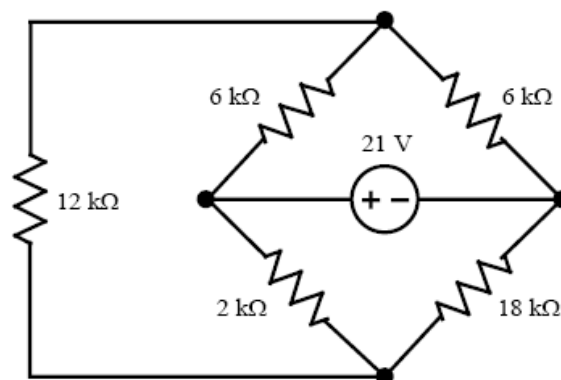
Problem 2.72

Find the power absorbed by the network shown.



Suggested Solution

Redrawing the network:

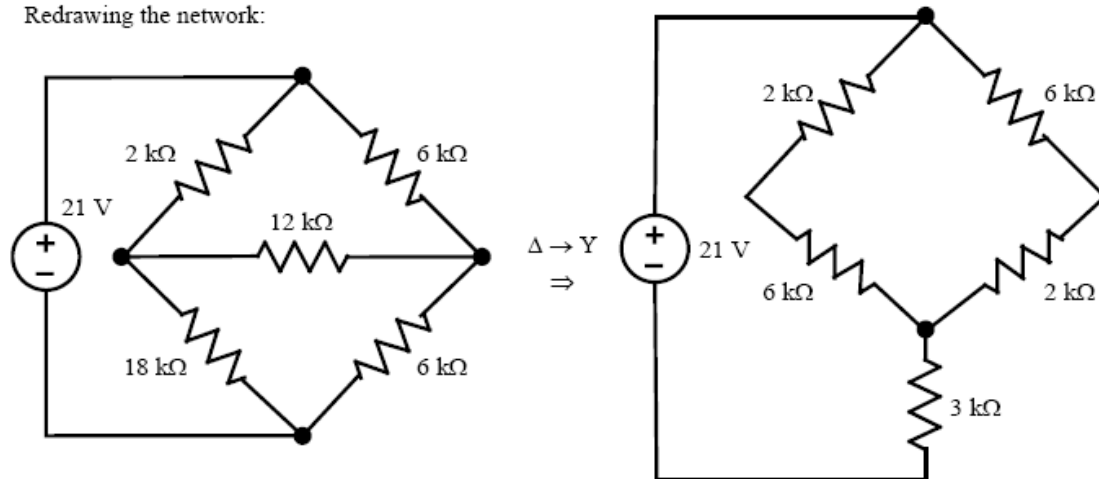

The equivalent resistance seen by the source is:


$$\begin{aligned} R_{eq} &= \left[(2 \text{ k}\Omega + 6 \text{ k}\Omega) \parallel (6 \text{ k}\Omega + 2 \text{ k}\Omega) \right] + 3 \text{ k}\Omega \\ &= 4 \text{ k}\Omega + 3 \text{ k}\Omega \\ &= 7 \text{ k}\Omega \end{aligned}$$

Then,

$$P = \frac{(21 \text{ V})^2}{R_{eq}} = \frac{441}{7000} = 63 \text{ mW}$$


Problem 2.73

Find I_o in the circuit shown.

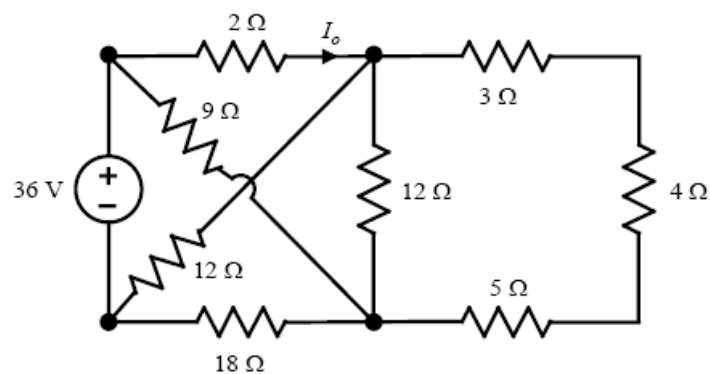

Suggested Solution

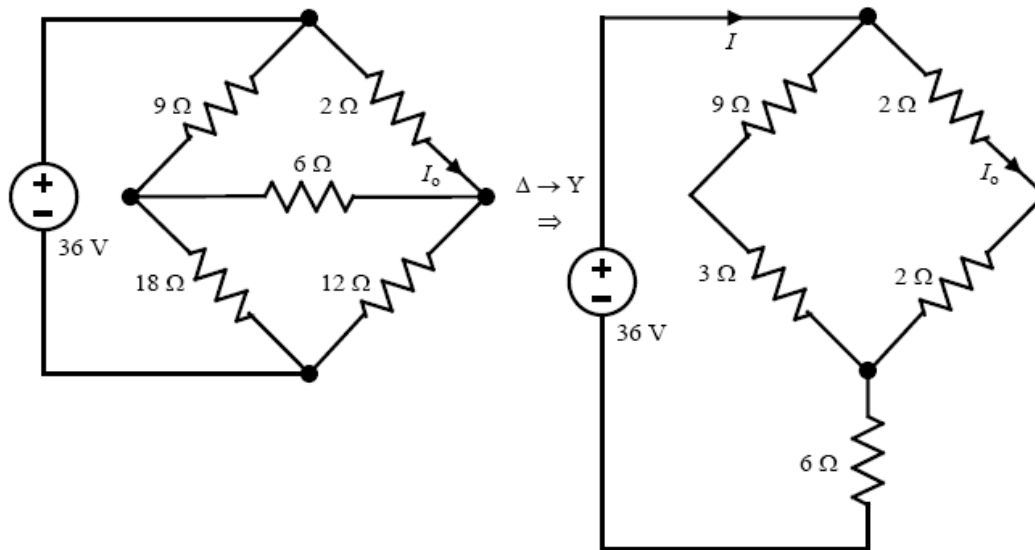Note that the four right-most resistors can be combined as $(3\ \Omega + 4\ \Omega + 5\ \Omega) \parallel 12\ \Omega = 6\ \Omega$. Then the circuit can be redrawn as:




$$I = \frac{36\text{ V}}{[(9\ \Omega + 3\ \Omega) \parallel (2\ \Omega + 2\ \Omega)] + 6\ \Omega} = 4\text{ A}$$


$$I_o = \left[\frac{(9+3)}{(9+3)+(2+2)} \right] I = 3\text{ A}$$

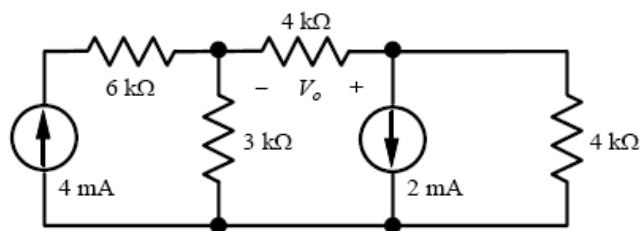Problem 3.4

Use nodal analysis to find V_o in the circuit shown.



Suggested Solution

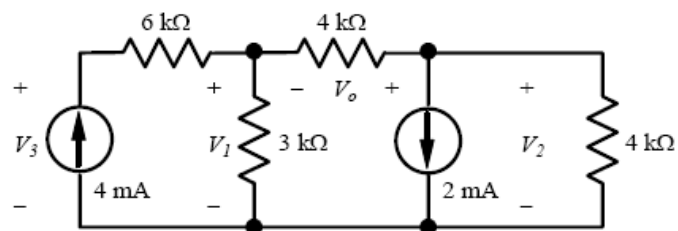

$$\frac{V_3 - V_1}{6 \text{ k}\Omega} = 4 \text{ mA}$$

$$\frac{V_1 - V_3}{6 \text{ k}\Omega} + \frac{V_1}{3 \text{ k}\Omega} + \frac{V_1 - V_2}{4 \text{ k}\Omega} = 0$$

$$\frac{V_2 - V_1}{4 \text{ k}\Omega} + \frac{V_2}{4 \text{ k}\Omega} = -2 \text{ mA}$$

In matrix form:


$$\begin{bmatrix} -\frac{1}{6000} & 0 & \frac{1}{6000} \\ \frac{1}{6000} + \frac{1}{3000} + \frac{1}{4000} & -\frac{1}{4000} & -\frac{1}{6000} \\ -\frac{1}{4000} & \frac{1}{4000} + \frac{1}{4000} & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0.004 \\ 0 \\ -0.002 \end{bmatrix} \Rightarrow \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 6.5455 \\ -0.7273 \\ 30.5455 \end{bmatrix}$$

$$\therefore V_o = V_2 - V_1 = -0.73 - 6.55 = -7.28 \text{ V}$$


Alternately, since we know the current through the $6 \text{ k}\Omega$ resistor is 4 mA , we know that $V_3 = V_1 + 24 \text{ V}$. Therefore, we really need only 2 equations to solve this problem. Those are:

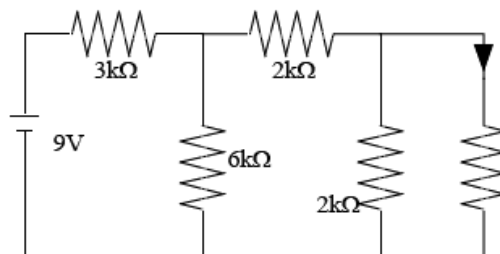Problem 3.5

Find I_o in the circuit using nodal analysis



Suggested Solution

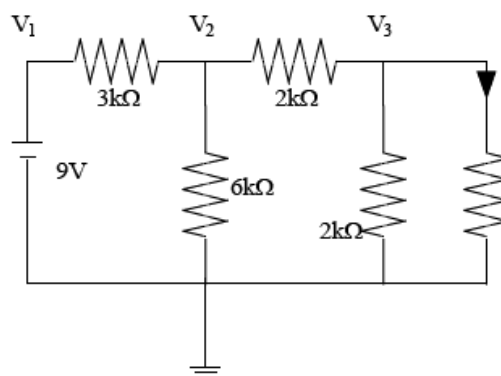

$$V_1 = 9V$$

$$\frac{9 - V_2}{3k} = \frac{V_2}{6k} + \frac{V_2 - V_3}{2k}$$


$$\frac{V_3 - V_2}{2k} + \frac{V_3}{2k} + \frac{V_3}{2k} = 0 \Rightarrow V_3 = 1.2V, I_0 = \frac{1.2}{2k} = 0.6mA$$

$$V_3 = 1.2V$$


$$I_0 = 0.6mA$$

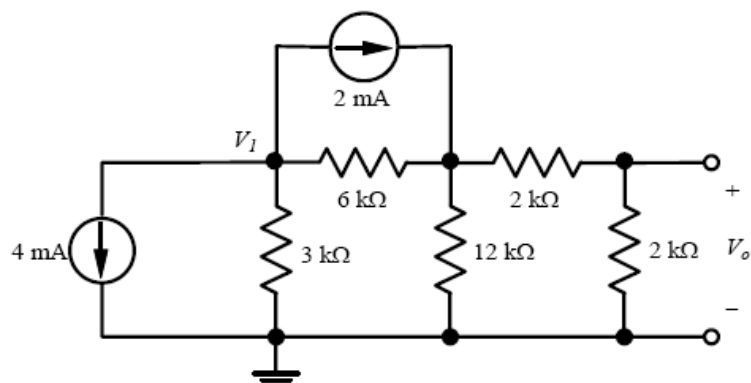Problem 3.6

Use nodal analysis to find both V_1 and V_o in the circuit shown.



Suggested Solution

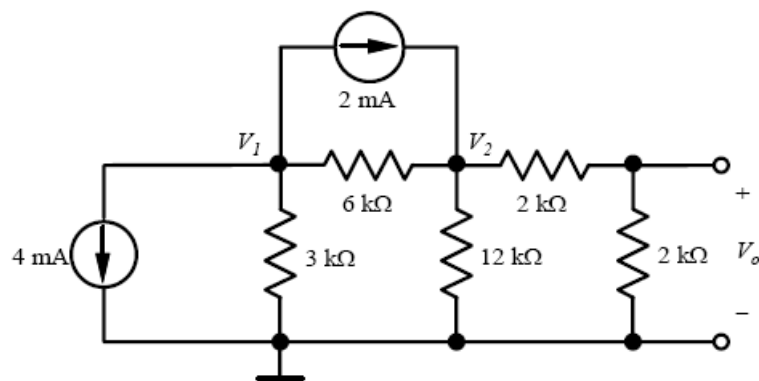

$$\frac{V_1}{3 \text{ k}\Omega} + \frac{V_1 - V_2}{6 \text{ k}\Omega} = -4 \text{ mA} - 2 \text{ mA}$$

$$\frac{V_2 - V_1}{6 \text{ k}\Omega} + \frac{V_2}{12 \text{ k}\Omega} + \frac{V_2}{2 \text{ k}\Omega + 2 \text{ k}\Omega} = 2 \text{ mA}$$


In matrix form:

$$\begin{bmatrix} \frac{1}{3000} + \frac{1}{6000} & -\frac{1}{6000} \\ -\frac{1}{6000} & \frac{1}{6000} + \frac{1}{12000} + \frac{1}{4000} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -0.006 \\ 0.002 \end{bmatrix} \Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -12 \\ 0 \end{bmatrix}$$


$$\therefore V_1 = -12 \text{ V and } V_o = \frac{2000}{2000 + 2000} V_2 = 0 \text{ V}$$

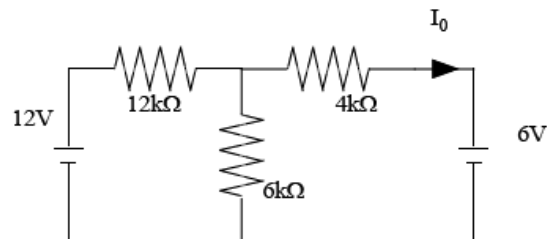Problem 3.8

Find I_0 in the network using nodal analysis



Suggested Solution

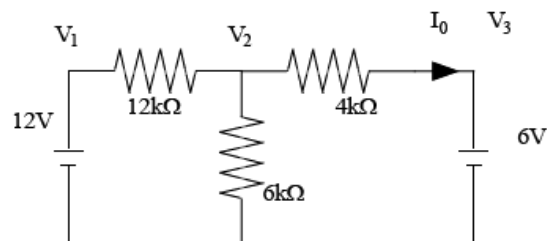

$$V_1 = 12\text{V}; V_3 = -6\text{V}$$


$$\frac{V_2 - 12}{12\text{K}} + \frac{V_2}{6\text{k}} + \frac{V_2 + 6}{4\text{k}} = 0 \Rightarrow V_2 = -1\text{V}$$

$$V_2 = -1\text{V}; I_0 = 1.25\text{mA}$$


$$I_0 = \frac{V_2 - V_3}{4\text{k}} = \frac{-1 + 6}{4\text{k}} = 1.25\text{mA}$$

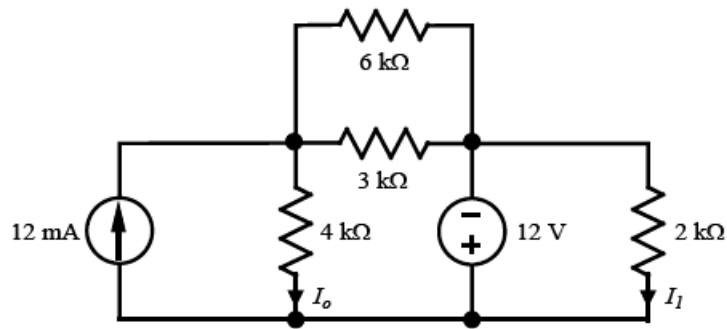Problem 3.10

Use nodal analysis to find I_o and I_1 in the circuit shown.



Suggested Solution

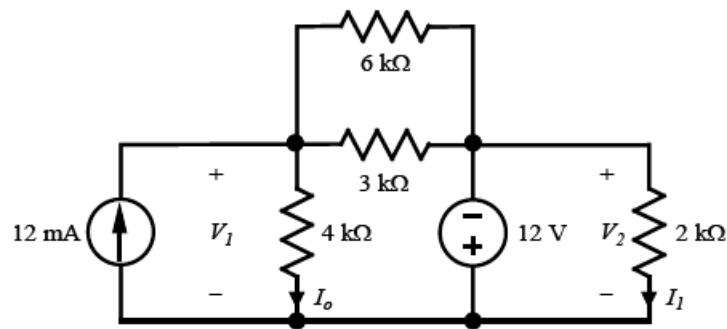


$$V_2 = -12 \text{ V} \Rightarrow I_1 = \frac{V_2}{2 \text{ k}\Omega} = \frac{-12}{2000} = -6 \text{ mA}$$

$$-12 \text{ mA} + \frac{V_1}{4 \text{ k}\Omega} + \frac{V_1 - (-12 \text{ V})}{6 \text{ k}\Omega} + \frac{V_1 - (-12 \text{ V})}{3 \text{ k}\Omega} = 0 \Rightarrow V_1 = 8 \text{ V} \Rightarrow I_o = \frac{V_1}{4 \text{ k}\Omega} = \frac{8}{4000} = 2 \text{ mA}$$


$$I_o = 2 \text{ mA}, I_1 = -6 \text{ mA}$$

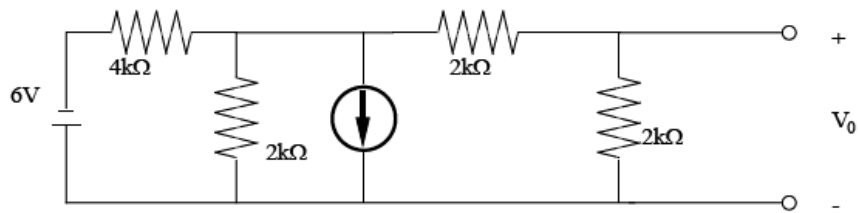Problem 3.12

Use nodal analysis to find V_0 in the network



Suggested Solution

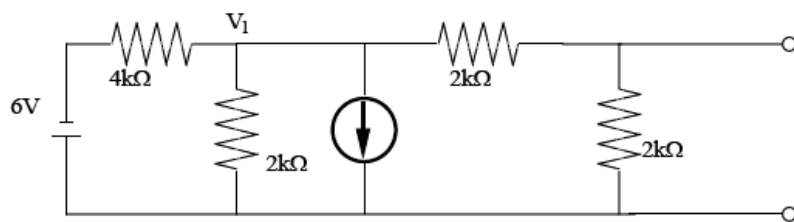

$$\frac{V_1 - (-6)}{4k} + \frac{V_1}{2k} + \frac{2}{k} + \frac{V_1}{2k + 2k} = 0$$

\Rightarrow


$$V_1 = \frac{-7}{2}V; \therefore V_0 = \frac{-7}{2} \left(\frac{2k}{2k + 2k} \right)$$

$$V_0 = \frac{-7}{4}V$$


$$V_1 = \frac{-7}{2}V$$
$$V_0 = \frac{-7}{4}V$$

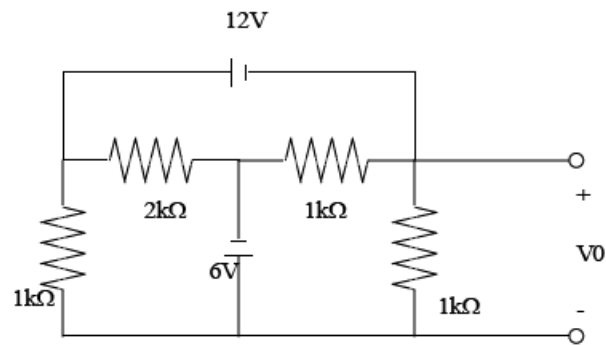Problem 3.22

Find V_0 in the circuit shown using Nodal Analysis



Suggested Solution

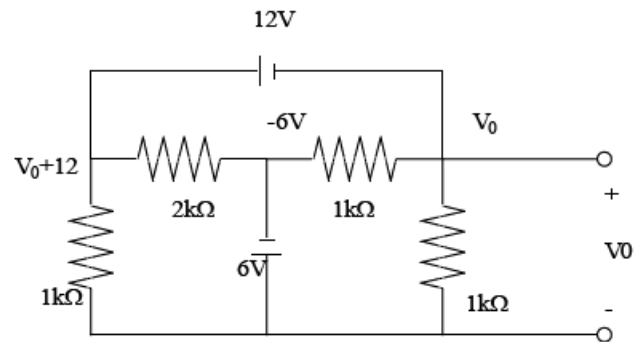

$$\frac{V_0 + 12}{1k} + \frac{V_0 + 12 + 6}{2k} + \frac{V_0 + 6}{1k} + \frac{V_0}{1k} = 0$$


$$V_0 \left(\frac{7}{2k} \right) = \frac{-27}{1k}$$

$$\therefore V_0 = -7.17V$$


$$V_0 = -7.17V$$

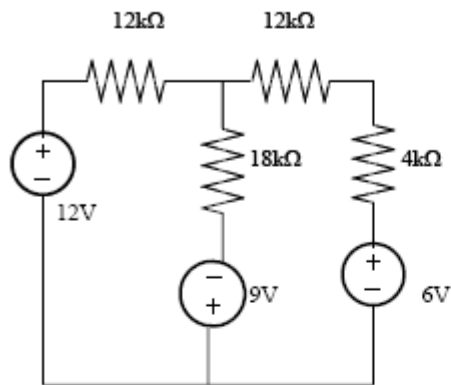Problem 3.26

Find the V_o in the circuit shown using nodal analysis.



Suggested Solution

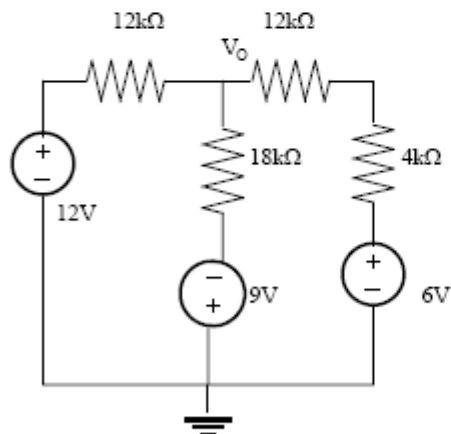


$$\frac{V_o - 12}{12K} + \frac{V_o + 9}{18K} + \frac{V_o + 6}{16K} = 0$$

$$V_o \left(\frac{1}{12} + \frac{1}{18} + \frac{1}{16} \right) = 0.621V$$


$$V_o = 0.621V$$

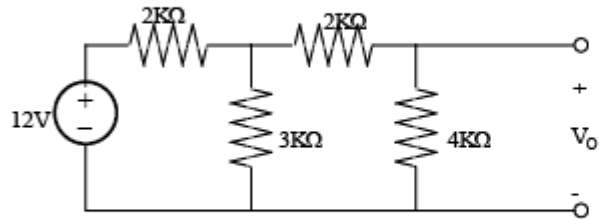Problem 3.42

Use mesh equations to find V_o in the circuit shown.



Suggested Solution

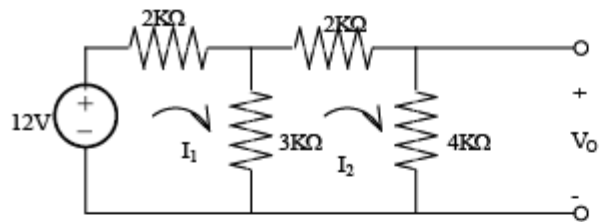

$$\begin{bmatrix} 5K & -3K \\ -3K & 4K \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5K & -3K \\ -3K & 4K \end{bmatrix}^{-1} \begin{bmatrix} 12 \\ 0 \end{bmatrix}$$


$$V_o = 4V$$

$$I_2 = \frac{1}{K} A$$


$$V_o = 4V$$

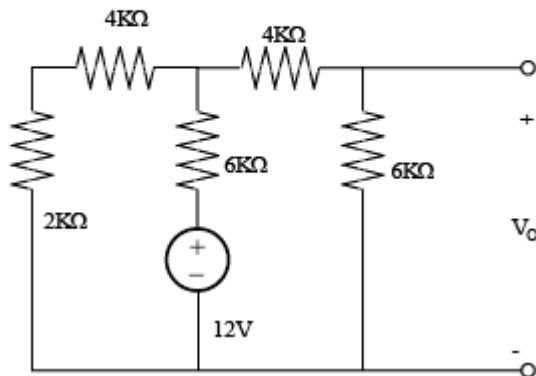Problem 3.44

Use mesh analysis to find V_o in the circuit shown.



Suggested Solution

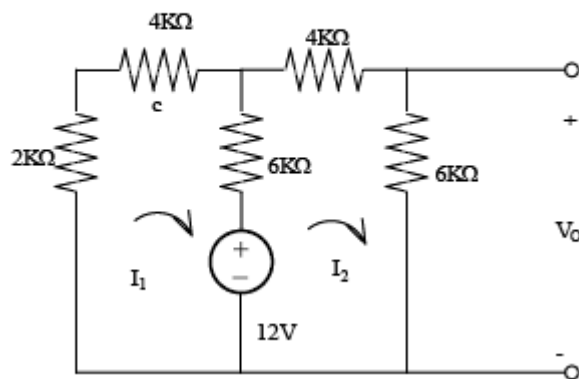

$$\begin{bmatrix} 12K & -6K \\ -6K & 12K \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -12 \\ 12 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 12K & -6K \\ -6K & 12K \end{bmatrix}^{-1} \begin{bmatrix} -12 \\ 12 \end{bmatrix}$$


$$I_2 = \frac{2}{3} \text{ mA}$$

$$V_o = \frac{4}{3} \text{ V}$$


$$V_o = \frac{4}{3} \text{ V}$$

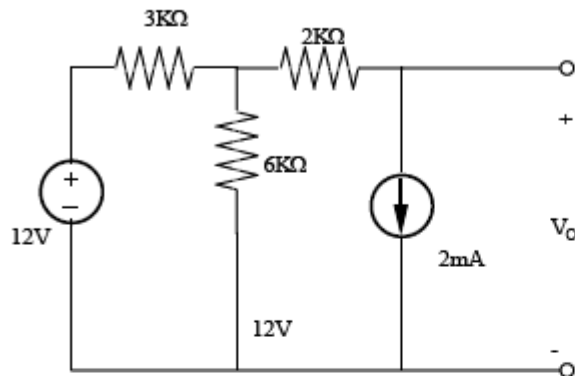Problem 3.45

Use mesh analysis to find V_o in the network shown.



Suggested Solution

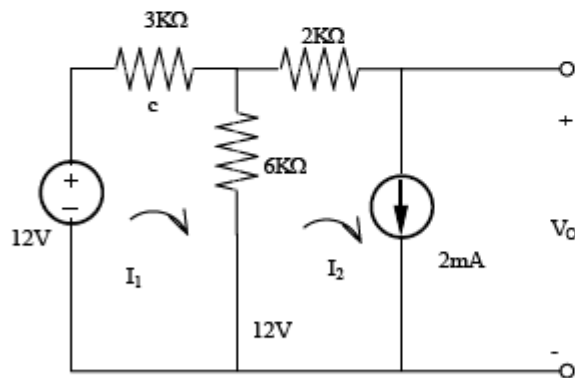

$$-12 + 3KI_1 + K(I_1 - I_2) = 0$$

$$I_2 = \frac{2}{K}$$


$$I_1 = \frac{8}{3K}$$

$$-12 + 3K\left(\frac{8}{3K}\right) + 2K\left(\frac{2}{K}\right) = V_o = 0V$$


$$V_o = 0V$$

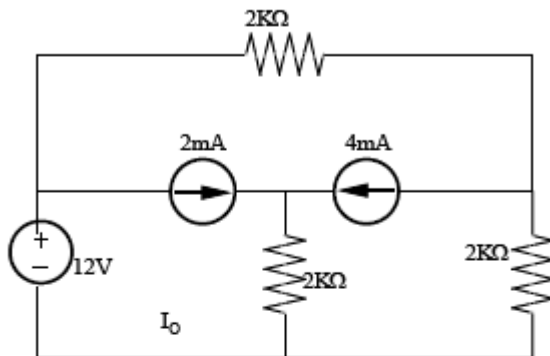Problem 3.47

Use loop analysis to find I_0 in the circuit shown.



Suggested Solution

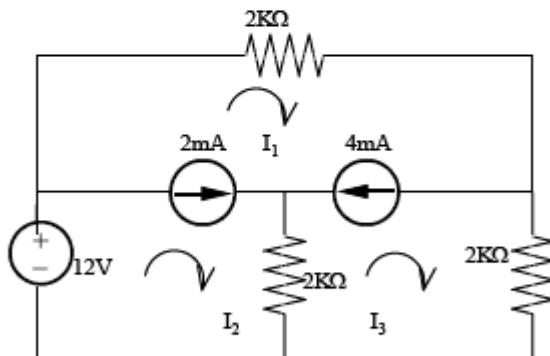

$$12 = 2KI_2 + 2KI_3$$

$$I_1 - I_2 = \frac{2}{K}$$


$$I_2 - I_3 = \frac{4}{K}$$

$$I_1 = I_0 = 7mA$$


$$I_1 = I_0 = 7mA$$

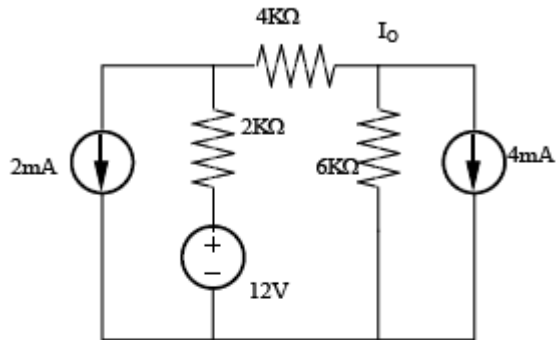Problem 3.49

Find I_o in the network shown using mesh analysis.



Suggested Solution

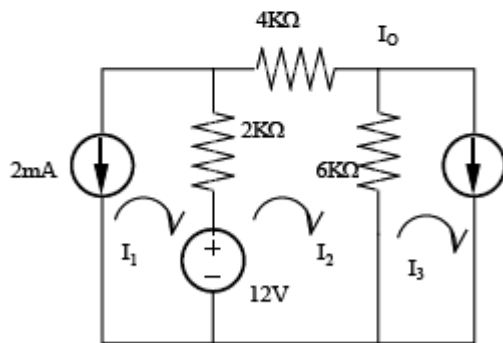

$$I_1 = \frac{-2}{K}$$

$$I_3 = \frac{4}{K}$$

$$-12 + 2K(I_2 - I_1) + 4KI_2 + 6K(I_2 - I_3) = 0$$


$$I_2 = \frac{16}{6} mA$$

$$I_o = I_2 = 2.67 mA$$


$$I_o = I_2 = 2.67 mA$$

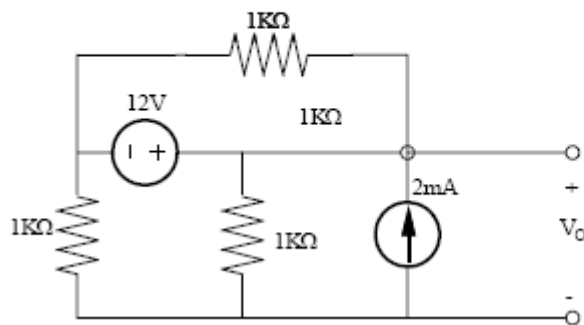Problem 3.51

Find V_o in the circuit shown using mesh analysis.



Suggested Solution

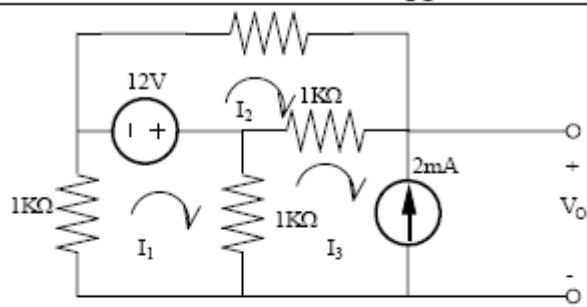

$$2KI_1 - 1KI_3 = -12$$

$$2KI_2 - 1KI_3 = 12$$

$$I_3 = \frac{-2}{K}$$

\Rightarrow

$$2KI_1 + 2 = -12$$

$$2KI_2 + 2 = 12$$

$$I_1 = \frac{-7}{K}, I_2 = \frac{5}{K}$$


$$V_o = \frac{7}{K}(1K) - \frac{5}{K}(1K) = 2V$$

$$V_o = 2V$$


$$V_o = 2V$$

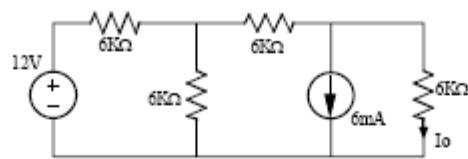Problem 4.5

In the network shown find I_o using superposition




Suggested Solution

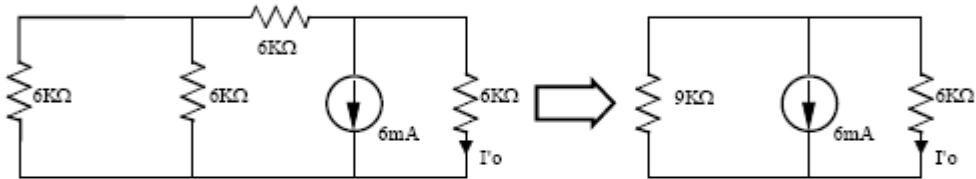

Zero the indep. voltage source
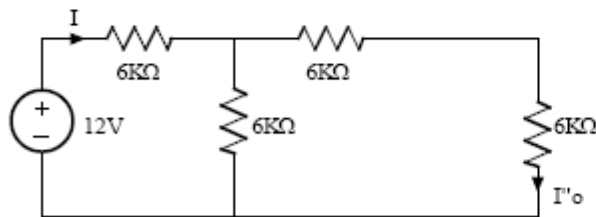
$$I'_o = -0.006 \left(\frac{9K}{9K+6K} \right) = -\frac{18}{5} \text{ mA}$$



Zero the indep. current source


$$I = \frac{12}{6K+6K \left(\frac{6K}{6K+6K} \right)} = \frac{6}{5} \text{ mA}$$

$$I''_o = I \left(\frac{6K}{6K+12K} \right) = \frac{2}{5} \text{ mA}$$

$$I_o = I'_o + I''_o = \left(-\frac{18}{5} + \frac{2}{5} \right) \text{ mA} = -\frac{16}{5} \text{ mA}$$

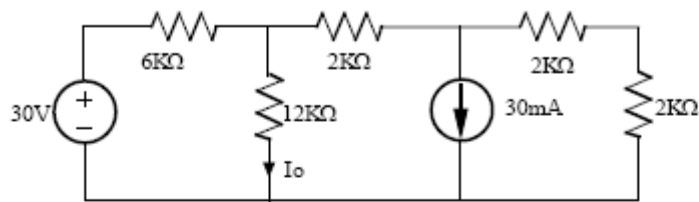
Problem 4.6

Find I_o in the circuit shown using superposition




Suggested Solution

Zero the indep. current source

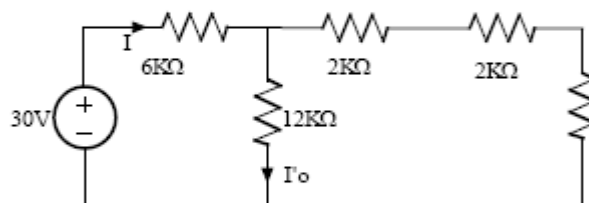

$$I = \frac{30}{6K + 12K \parallel 6K} = 3mA, \quad I'o = I \frac{6K}{18K} = 1mA$$

Zero the indep. voltage source

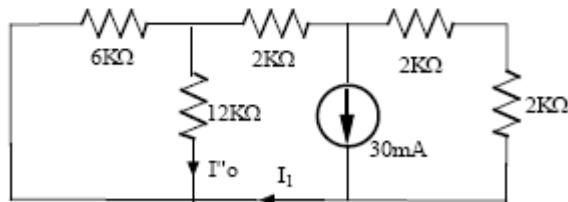

$$I_1 = 0.03 \left(\frac{4K}{4K + 2K + 6K \parallel 12K} \right) = 12mA$$


$$I''o = -0.012 \left(\frac{6K}{18K} \right) = -4mA$$

$$\boxed{I_o = I'o + I''o = 3mA}$$


~

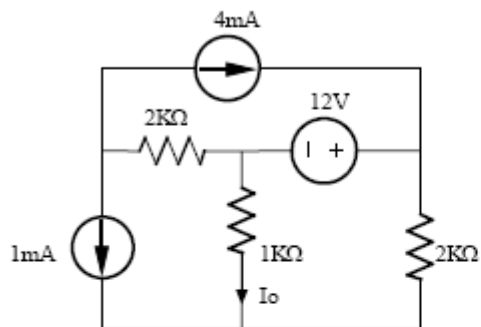Problem 4.16


Find I_o in the network shown using superposition.




Suggested Solution

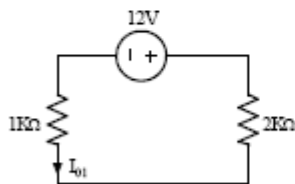

I_o due to 12V source

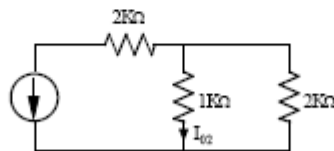

I_o due to 1mA source

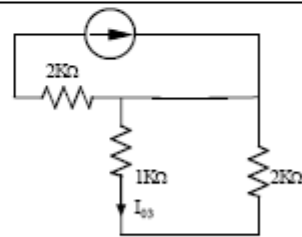

I_o due to 4mA source

$$I_{o1} = -12/(1K+2K) = -4mA$$


$$I_{o2} = 2m[2K/(2K+3K)] = -1.33mA$$

$$I_{o3} = 0A$$


$$I_o = I_{o1} + I_{o2} + I_{o3} = -5.33mA$$

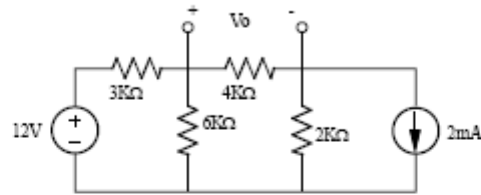Problem 4.32

Use Thevenin's Theorem to find V_o in the network shown.





Suggested Solution

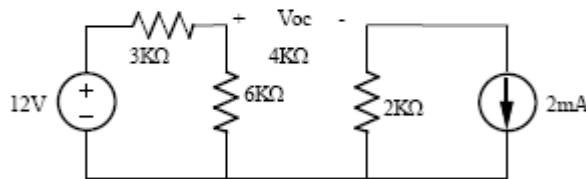


$$V_{oc} = 12 \left(\frac{6K}{9K} \right) + 2m \cdot 2K = 12V$$

$$R_{th} = 3K \parallel 6K + 12K = 4K$$

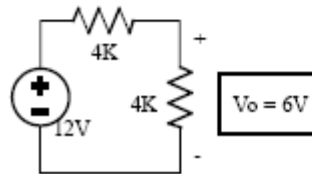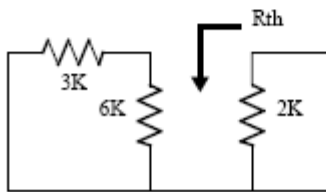


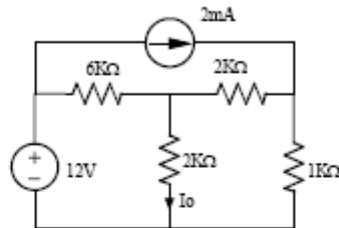Problem 4.34

Use Thevenin's Theorem to find I_o in the network shown.





Suggested Solution

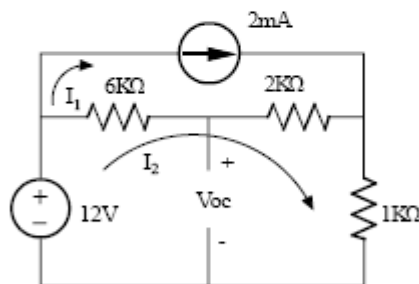


$$\begin{aligned} I_1 &= 2\text{mA} \\ -I_2 + 6K(I_2 - 2\text{m}) + 2K(I_2 - 2\text{m}) + 1K I_2 &= 0 \\ I_2 &= 28 / 9 \text{ mA} \end{aligned}$$

$$\text{Then } V_{oc} = 12 - 6K(I_2 - 2\text{m}) = 16 / 3 \text{ V}$$

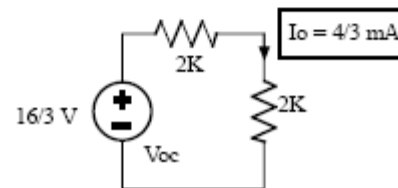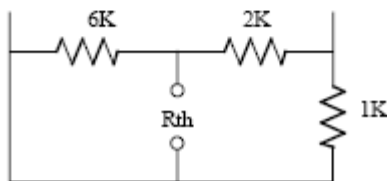


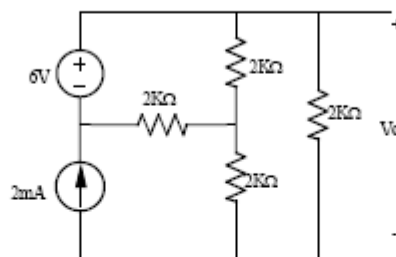Problem 4.40


Find V_o in the circuit shown using Thevenin's Theorem.



Suggested Solution

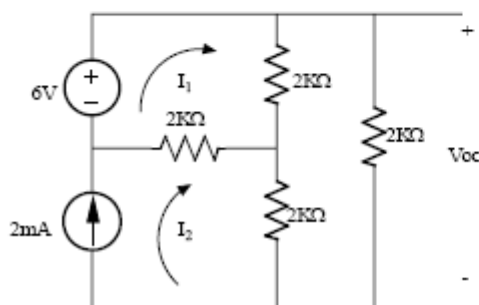


$$\begin{aligned} I_2 &= 2\text{m} \\ -6 + 4K I_1 + 2K(I_1 - 2\text{m}) &= 0 \\ I_1 &= 10/6K = 5/3 \text{ mA} \\ V_{oc} &= 4K I_1 + 2K I_2 = 4K(5/3\text{m}) + 2K 2\text{m} = 32/3 \text{ V} \end{aligned}$$

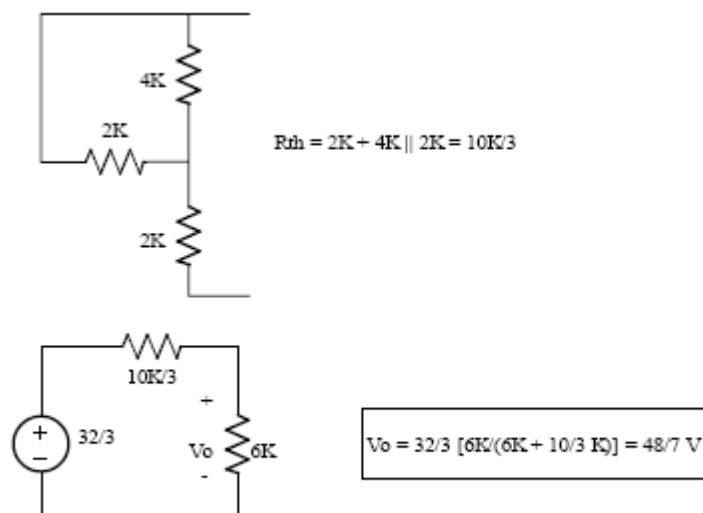


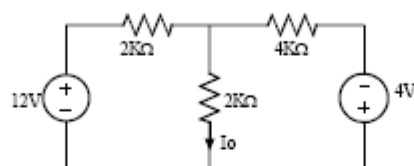Problem 4.62

Find I_o in the network shown using Norton's Theorem




Suggested Solution

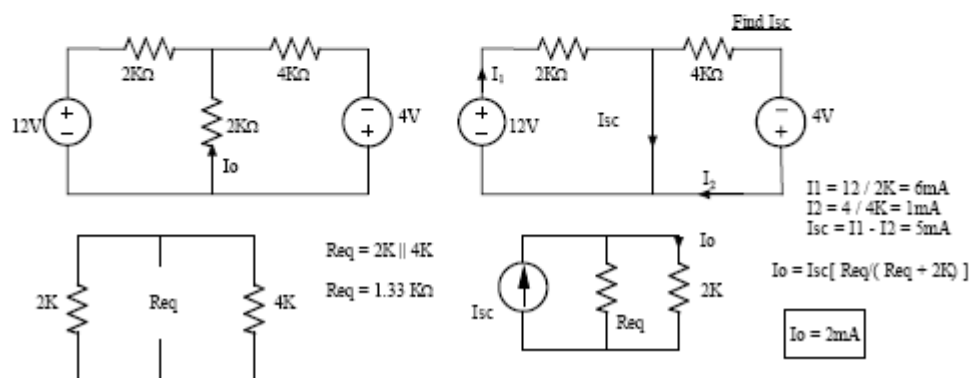


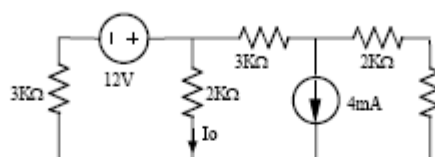Problem 4.63

Use Norton's Theorem to find I_o in the circuit shown.




Suggested Solution

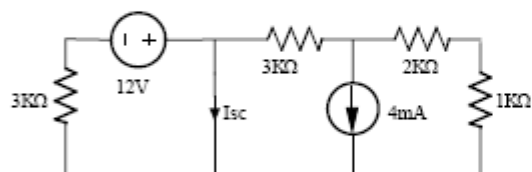


$$I_{sc} = 12 / 3K - 4m[3K / (3K + 3K)]$$

$$I_{sc} = 2mA$$

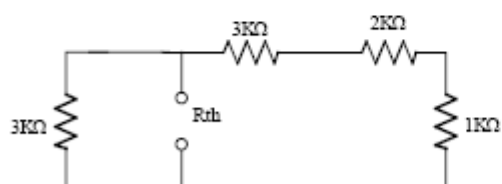


$$R_{th} = 3K \parallel 6K = 2K\Omega$$

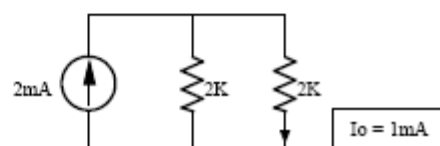


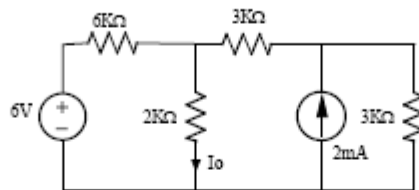Problem 4.64

Find I_o in the network shown using Norton's Theorem.




Suggested Solution

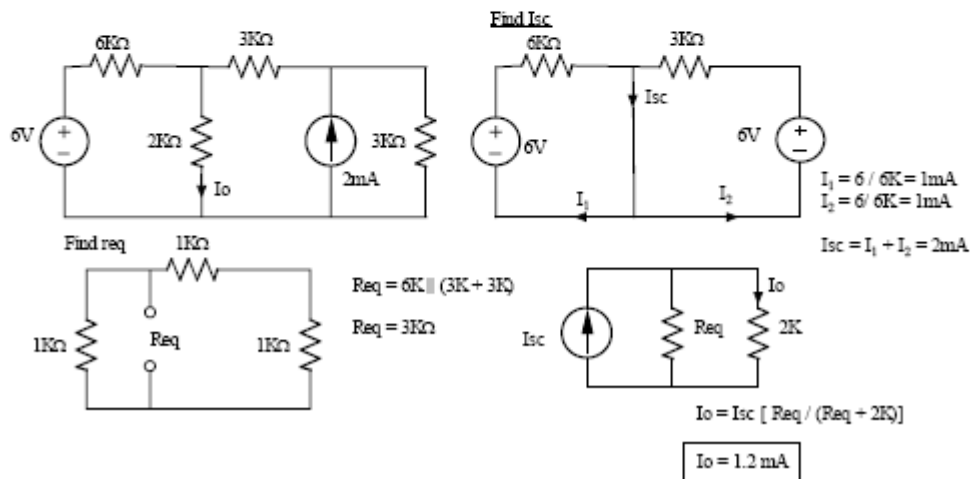


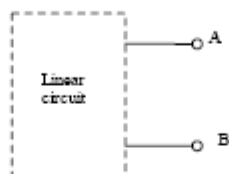Problem 4.69

If an $8\text{-K}\Omega$ load is connected to the terminals of the network shown, $V_{AB} = 16\text{V}$. If a $2\text{-K}\Omega$ load is connected to the terminals $V_{AB} = 8\text{V}$. Find V_{AB} if a $20\text{K}\Omega$ load is connected to the terminals.



Suggested Solution

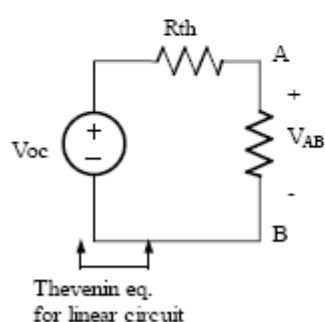

$$V_{AB} = V_{oc} [R_L / (R_L + R_{th})] \Rightarrow V_{oc} = V_{AB} [1 + R_{th} / R_L]$$

$$\text{If } R_L = 8\text{K}\Omega, V_{AB} = 16\text{V} \Rightarrow V_{oc} = 16 [1 + R_{th} / 8\text{K}]$$

$$\text{If } R_L = 2\text{K}\Omega, V_{AB} = 8\text{V} \Rightarrow V_{oc} = 8 [1 + R_{th} / 2\text{K}]$$

$$\text{yield: } R_{th} = 4\text{K}\Omega \text{ and } V_{oc} = 24\text{V}$$

$$\text{If } R_L = 20\text{K}\Omega, V_{AB} = 24 [20 / (20 + 4)]$$

$V_{AB} = 20\text{ V}$